

Color: IVORY

University of Arizona  
Department of Electrical & Computer Engineering

ECE 220      Basic Circuits

# Examination 2

March 3, 2005

Closed book/notes, calculators allowed up to level of TI89, HP48.

**Part I: 6 questions    Part II: 6 questions.**

**Part II is worth twice as much as Part I.    18 POINTS TOTAL**

On the SCANTRON write and bubble-in your:

1. **Name** (Last, first)
2. **1-3 digit ID number** which was given to you at the first exam. Write this left-justified under columns A-C under IDENTIFICATION NUMBER.
3. Write the **color of your exam paper** (IVORY or GREEN) on the top left margin of the SCANTRON.

Place your UA picture ID card on the adjacent desk where it can be easily seen.

When the 9:30 bell rings, begin the examination. All work should be done on the examination paper. Allow for reasonable amounts of roundoff error, and **carefully** mark one choice for each problem on the SCANTRON answer sheet.

e.g. 1    


A	B	C	D	E
①	②	●	④	⑤

 if the answer for Question 1 is C.

All SCANTRON forms and examinations will be collected at or before 10:30. You will be asked to stop writing and hand in your papers/answer sheets. **Failure to comply promptly may result in disqualification from the exam.**

NAME:           RNS          

SIGNATURE:           SOLUTIONS          

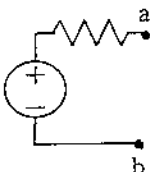

Use this template for the polarity of Thevenin/Norton equivalent ckts with respect to terminals a-b

Write your ECE 220 ID number here and on the SCANTRON:

\_\_\_\_\_


Part I

~10 min

*5mA, 3kΩ are in parallel with 9V source & so don't affect Thev params.*

1. The parameters of the Thevenin equivalent circuit at terminals a-b are:

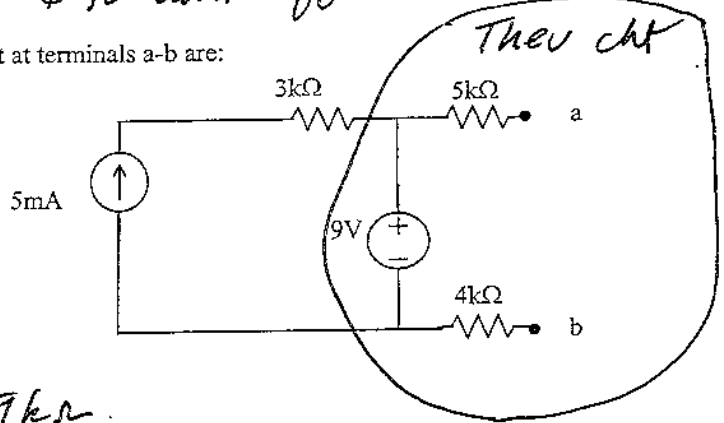- (a)  $V_{Th} = 9V, R_{Th} = 9k\Omega$
- (b)  $V_{Th} = 24V, R_{Th} = 9k\Omega$
- (c)  $V_{Th} = -6V, R_{Th} = 12k\Omega$
- (d)  $V_{Th} = 9V, R_{Th} = 2.25k\Omega$
- (e) None of these




*Also, Method 2 easily shows that  $V_{Th} = 9V$  &  $R_{Th} = 5 + 4 = 9k\Omega$ .*

2. Identify one element that has no effect on the node voltages in this ckt.

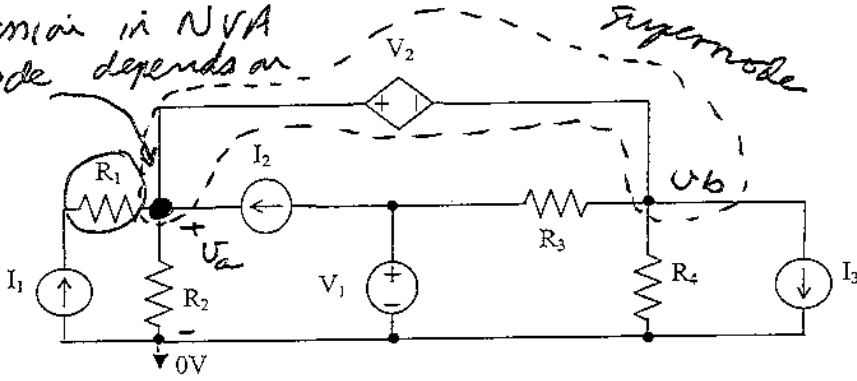- (a)  $I_1$
- (b)  $I_2$
- (c)  $R_1$
- (d)  $R_2$
- (e)  $V_2$

*KCL expression in NVA at this node depends on  $I_1$  but not on  $R_1$ .*




*ie.*

$$\frac{V_a}{R_1} + \frac{V_b - V_a}{R_3} + \frac{V_b}{R_4} = I_1 + I_2 - I_3$$

3. What is the voltage  $v_x$  dropped across the  $10\Omega$  resistor?

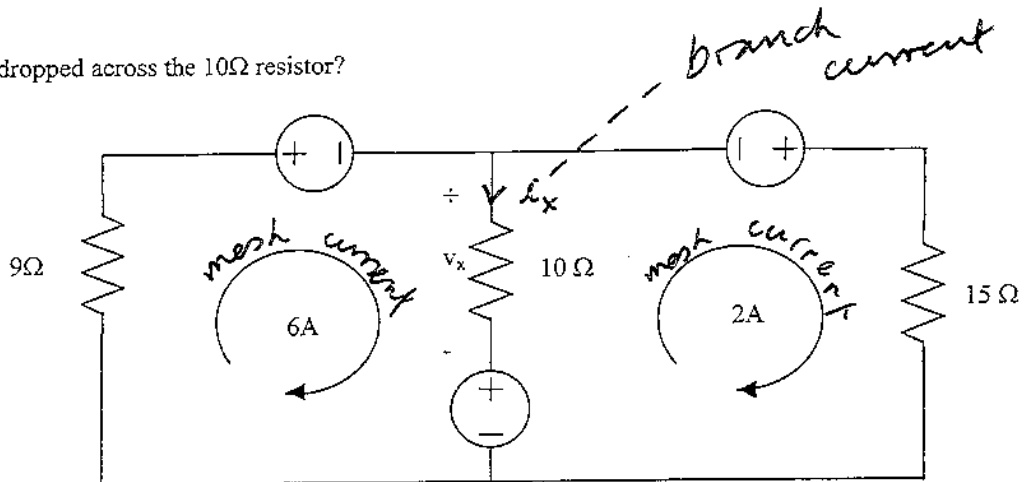- (a) 60V
- (b) -40V
- (c) -80V
- (d) 40V
- (e) None of these





$$V_x = 10 i_x = 10(6 - 2) = 40V$$

Part I 10 min


4. How much current ( $i_s$ ) would flow through the shunt wire (short ckt) in this ckt?

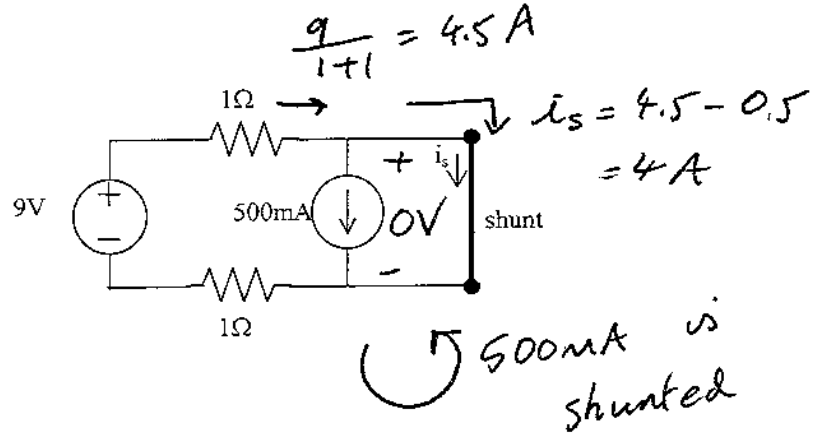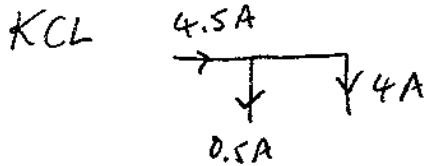- (a) -500mA
- (b) 4.5A
- (c) 4 A
- (d) 5A
- (e) None of these



5. A simplified equivalent circuit seen from the terminals marked • consists of:

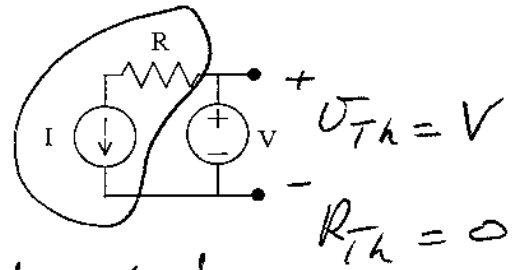
- (a) a current source (only)
- (b) a voltage source (only)
- (c) a voltage source in series with a resistor
- (d) a current source in parallel with a resistor



$I+R$  are in parallel with  $V$ , so are invisible to any load applied at the terminals.

6. A valid supermesh KVL equation for this ckt is given by:

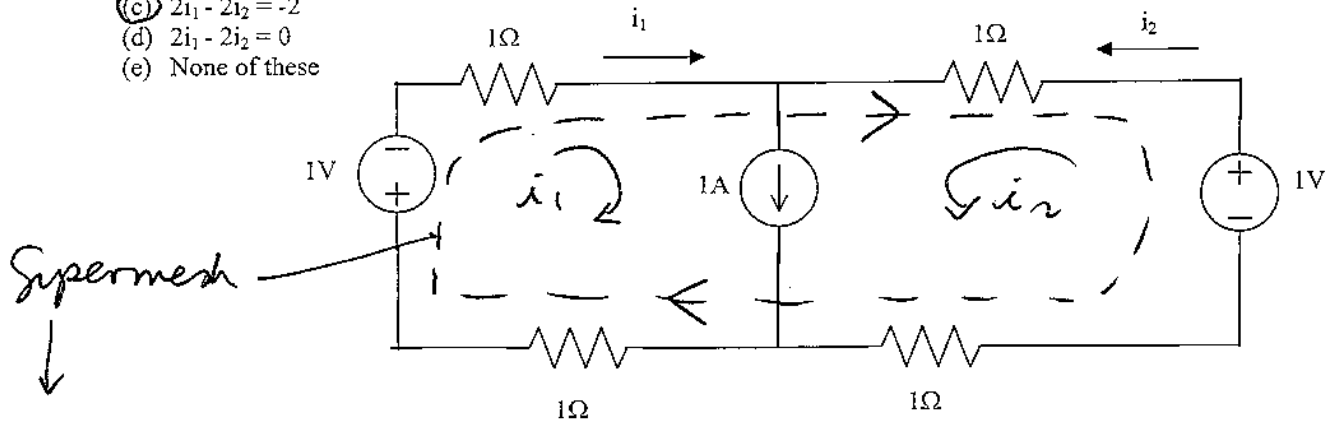- (a)  $2i_1 + 2i_2 = 2$
- (b)  $2i_1 + 2i_2 = -2$
- (c)  $2i_1 - 2i_2 = -2$
- (d)  $2i_1 - 2i_2 = 0$
- (e) None of these



KVL:


$$1 + (1)i_1 - (1)i_2 + 1 - (1)i_2 + (1)i_1 = 0$$

$$\therefore 2i_1 - 2i_2 = -2$$

Part II ~40 min

17. Find the parameters of the Thevenin equivalent ckt seen at terminals a-b.

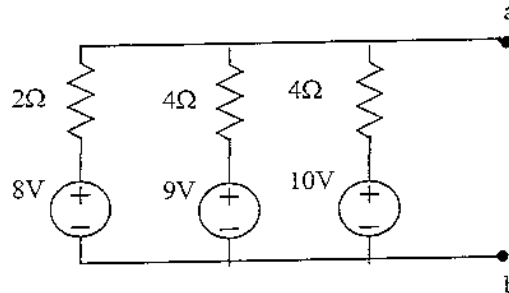- (a)  $V_{th} = 9V, R_{th} = 1\Omega$
- (b)  $V_{th} = 9V, R_{th} = 4\Omega$
- (c)  $V_{th} = 8.75V, R_{th} = 1\Omega$
- (d)  $V_{th} = 9.25V, R_{th} = 1\Omega$
- (e) None of these



Method 2 Set voltage sources to 0V i.e. short ckt  
 $R_{Th} = 2 \parallel 4 \parallel 4 = 2 \parallel 2 = 1\Omega$   
 Mem

Restore sources and find  $V_{Th} = V_{ab}$ .

NVA  $\frac{V_{Th} - 8}{2} + \frac{V_{Th} - 9}{4} + \frac{V_{Th} - 10}{4} = 0$

$\therefore 2V_{Th} - 16 + V_{Th} - 9 + V_{Th} - 10 = 0$

$\therefore 4V_{Th} = 35$

$\therefore V_{Th} = 8.75V$

$\therefore$  Answer is (c).

80

What is the power consumed by the 10V source?  $= 10 i_{10}$ .  
 $\therefore$  need to find  $i_{10}$ .

(a) 25W


(b) 8W

(c) 5W

(d) 10W

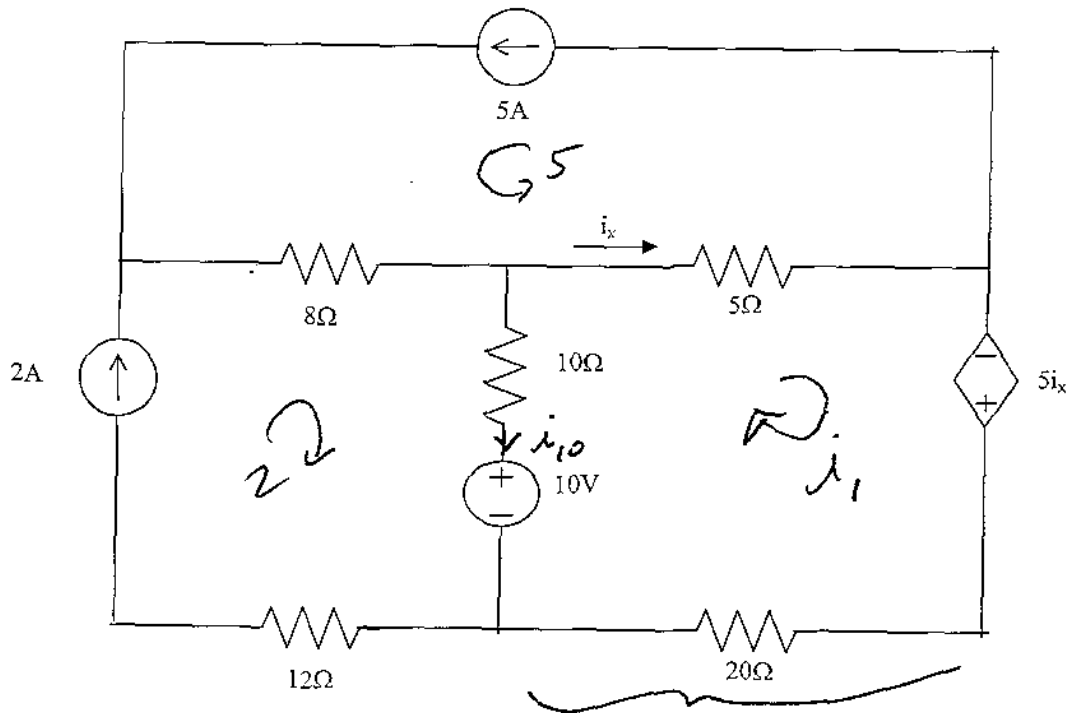(e) None of these

Only one unknown mesh current, so we use MCA.



KVL

$$-10 + 10(i_1 - 2) + 5(i_1 + 5) - 5i_x + 20i_1 = 0$$

C.E.  $i_x = 5 + i_1$

$$\therefore -10 + 10i_1 - 20 + 5i_1 + 25 - 25 - 5i_1 + 20i_1 = 0$$

$$30i_1 = 30$$

$$\therefore i_1 = 1 \text{ A}$$

$$\therefore i_{10} = 2 - i_1 = 2 - 1 = 1 \text{ A}$$


$$\therefore P_{10} = 10 i_{10} = 10 \text{ W}$$

9.

Find the power delivered by the 2A current source.  $= 2 \times V_1 = 2(5 - V_1)$

$\therefore$  find  $V_1$  using NVA.

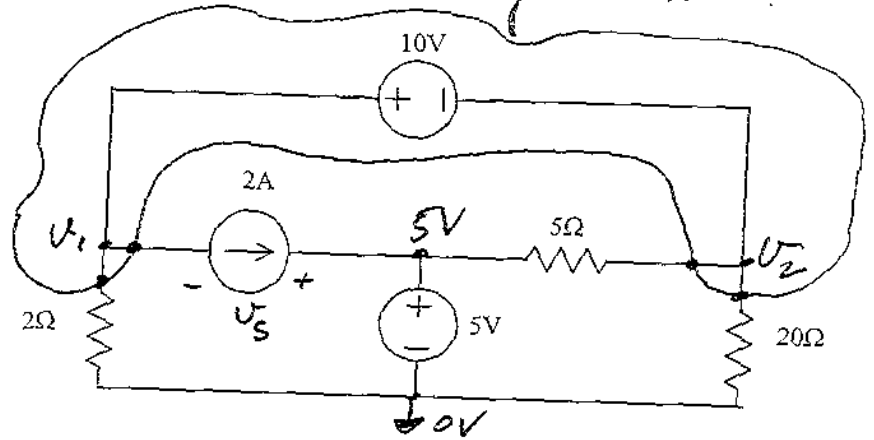- (a) 2.4W
- (b) 4W
- (c) 6W
- (d) -8W
- (e) None of these



NVA at supernode:

KCL  $\frac{V_1}{2} + 2 + \frac{V_2 - 5}{5} + \frac{V_2}{20} = 0$

$\therefore 10V_1 + 40 + 4V_2 - 20 + V_2 = 0$

$\therefore 10V_1 + 5V_2 = -20$  (1)

KVL  $\text{gnd} \rightarrow V_1 \rightarrow V_2 \rightarrow \text{gnd}$

$-V_1 + 10 + V_2 = 0 \Rightarrow -V_1 + V_2 = -10$  (2)

$\therefore$  (1) - 5 \* (2)  $\Rightarrow$

$10V_1 + 5V_2 = -20$


$-5V_1 + 5V_2 = -50$

$\frac{15V_1 + 0}{15V_1 + 0} = \frac{30}{30} \Rightarrow V_1 = 3V$

$\therefore P_{2A} = 2(5 - V_1) = 2 \times 3 = 6W.$

10. The equivalent resistance seen from the terminals marked • is:

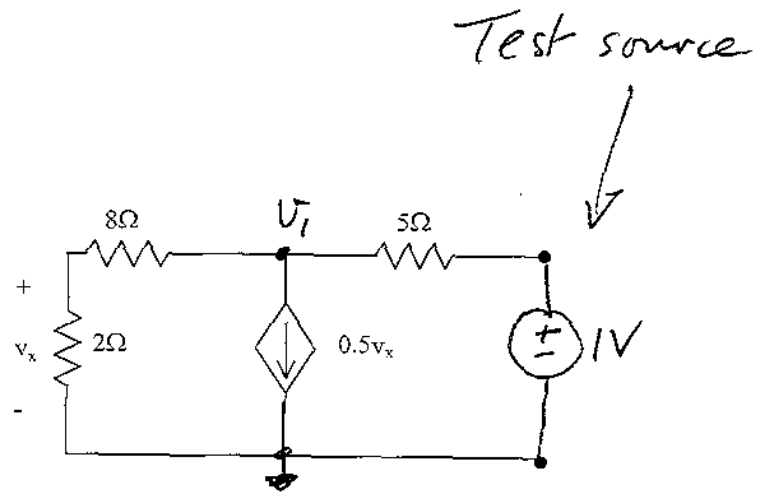- (a)  $2 \Omega$
- (b)  $3 \Omega$
- (c)  $6 \Omega$
- (d)  $10 \Omega$
- (e) None of these.



NVA @  $v_1$ -node:

$$\frac{v_1}{10} + 0.5 v_x + \frac{v_1 - 1}{5} = 0$$

V-Divider:

$$v_x = \left( \frac{2}{2+8} \right) v_1 = 0.2 v_1$$

$$\therefore 0.1 v_1 + 0.1 v_1 + 0.2 v_1 = 0.2$$

$$\therefore 0.4 v_1 = 0.2 \Rightarrow v_1 = 0.5 \text{ V}$$

$$\therefore \begin{array}{c} 0.5 \\ + \\ \text{---} 5\Omega \text{---} \\ | \\ \ominus 1\text{V} \\ | \\ - \end{array} \leftarrow i_T = \frac{1 - 0.5}{5} = 0.1 \text{ A}$$

$$\therefore R_{TH} = \frac{1\text{V}}{0.1\text{A}} = 10\Omega$$

11. Find the steady-state expression for  $v_o(t)$  in this AC ckt when  $i_s(t) = 100 \cos(10t - 45^\circ)$  mA.

(a)  $v_o(t) = 141.4 \cos(10t + 53.13^\circ)$  mV

(b)  $v_o(t) = 70.71 \cos(10t)$  mV


(c)  $v_o(t) = 70.71 \cos(10t + 53.13^\circ)$  mV

(d)  $v_o(t) = 200 \cos(10t - 45^\circ)$  mV

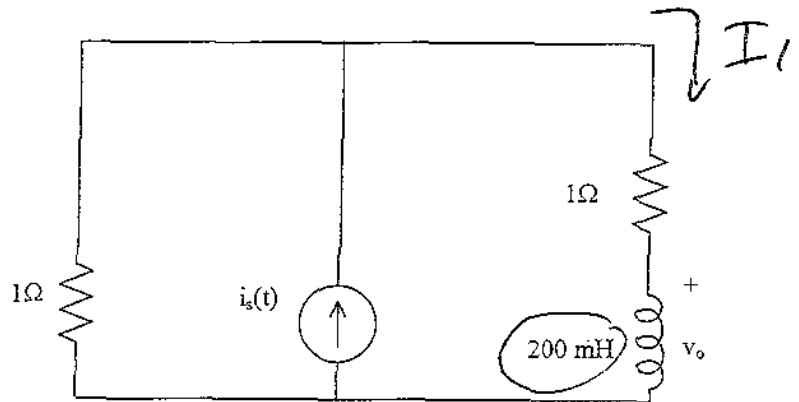(e) None of these.

Phasor current:

$$I_s = 100 \angle -45^\circ \text{ mA}$$



Apply current divider to find  $I_1$ .

$$j\omega L = j \cdot 10 \cdot 0.2 = j2\ \Omega$$

$$I_1 = \left( \frac{1}{1 + 1 + j2} \right) \cdot 100 \angle -45^\circ \text{ mA}$$

$$= \frac{100 \angle -45^\circ \text{ mA}}{2 + j2} = \frac{100 \angle -45^\circ \text{ mA}}{2\sqrt{2} \angle 45^\circ}$$



$$= \frac{50}{\sqrt{2}} \angle -90^\circ \text{ mA} = \frac{50}{\sqrt{2}} \times -j \text{ mA}$$

$$\therefore V_o = (j\omega L) I_1 = (j2) \times \left( \frac{50}{\sqrt{2}} \right) \times (-j) \text{ mV}$$

$$= \frac{100}{\sqrt{2}} (-j^2) \text{ mV} = \frac{100}{\sqrt{2}} \text{ mV} = 70.71 \text{ mV}$$

$$= 70.71 \angle 0^\circ \text{ mV}$$





$$\therefore \underline{V_o(t) = 70.71 \cos(10t) \text{ mV}}$$

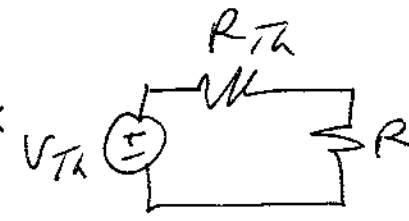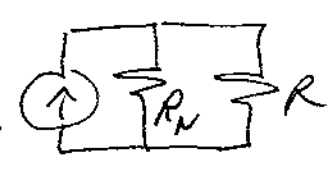Need to find:  $V_{Th}$    $\stackrel{OR}{=} i_N$  

12.

What is the maximum power that can be delivered to R, given that R can have any value?

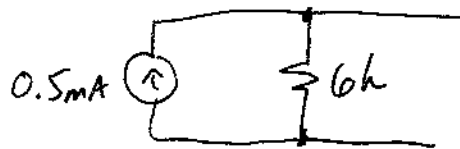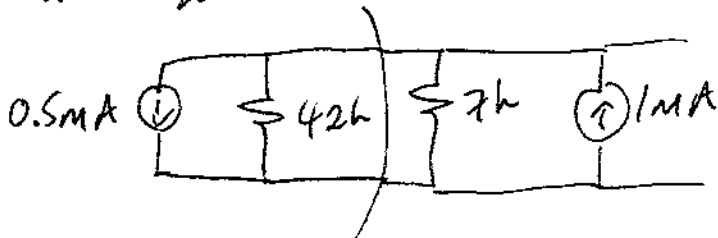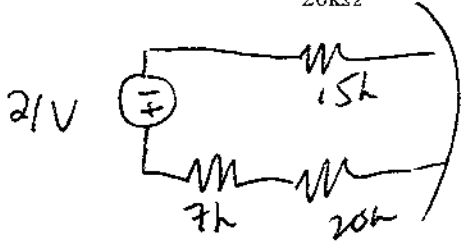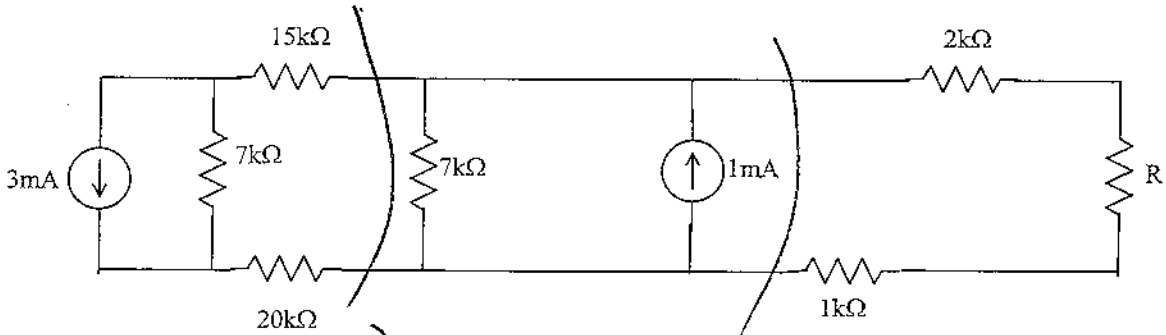- (a)  $250\mu W$  (b)  $300\mu W$  (c)  $220\mu W$  (d)  $100\mu W$  (e) None of these



$$\begin{aligned} \therefore p_{max} &= \frac{V_{Th}^2}{4R_{Th}} \\ &= \frac{3^2}{4 \times 9k} = 0.25mW \end{aligned}$$

