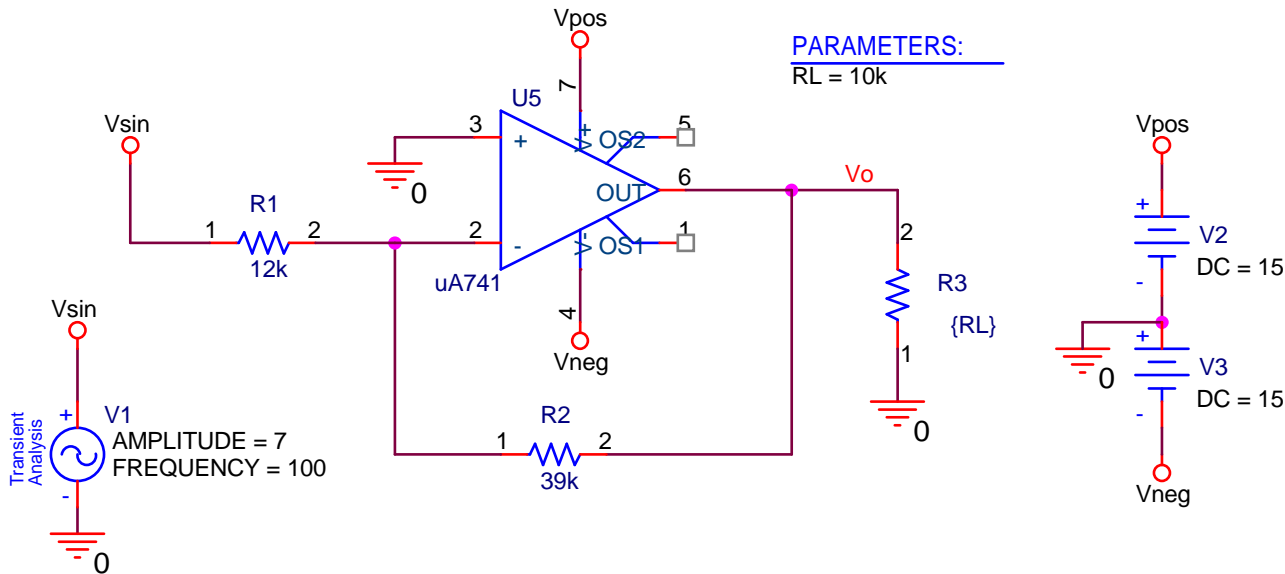


# Lecture 4 Goals:

- New PSpice Simulation:  
Time Domain (Transient)
- Ideal DC Voltage Source
- Difference Amplifier
- Light meter Design

# PART 1: Inverting Amplifier With Sinewave Input



## PSPICE:

*Analysis Type:*

*Time Domain (Transient)*

*Run to time: 20ms*

*Maximum step size: 1us*


*Parts:*

*VSIN/CLASS*

*uA741/EVAL*

- Run a Time Domain (Transient) with AMPLITUDE = {1, 3, 5, 7} Volts
- For AMPLITUDE = 1V and 7V do the following:
  - Label which waveform is input and which is output
  - Mark the peak for Input and Output
- For all amplitudes explain the form of the waveforms. Explain why some outputs are distorted.

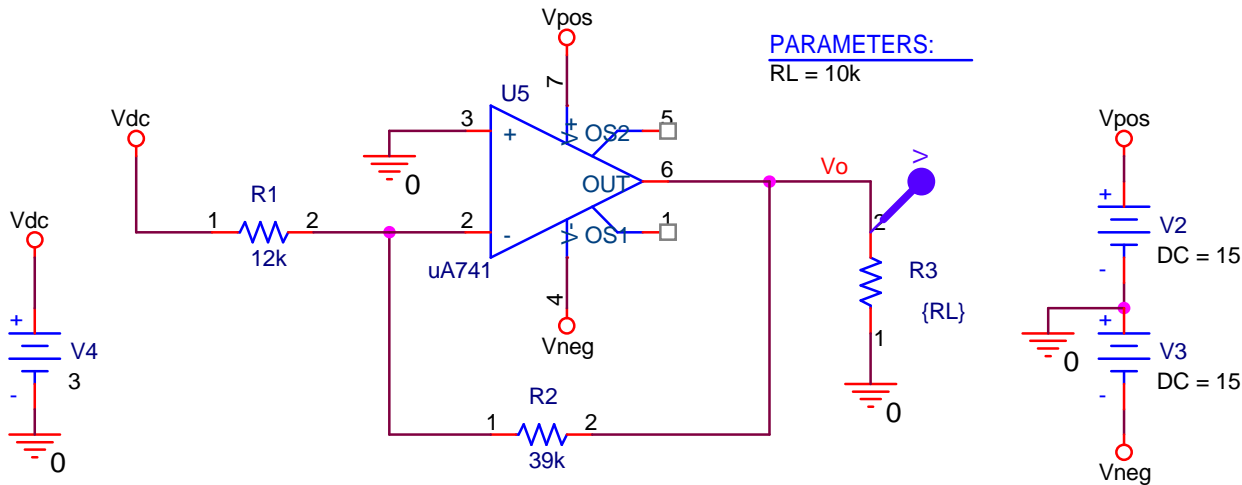
# PART 2: Inverting amplifier acting as an ideal DC voltage source



**PSPICE:**  
*Analysis Type: DC Sweep*  
*Global Parameter: RL*  
*Sweep Type: Linear*  
*Start Value: 50Ω*  
*End Value: 1kΩ*  
*Increment: 50Ω*

- Run a DC Sweep, sweeping the load resistance
- From the plot:
  - What is the value of this voltage source?
  - What is the range of RL over which it acts ideal?
  - Why is it acting ideal?

# PART 3: Difference Amplifier

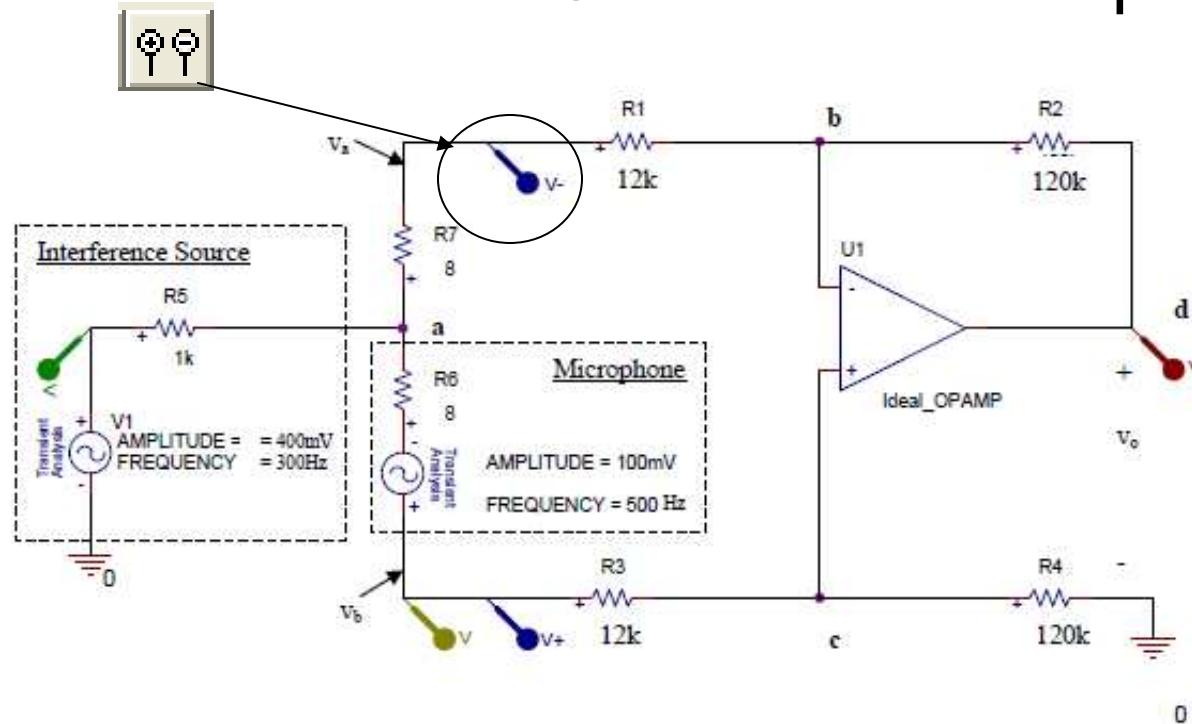


**PSPICE:**  
 Analysis Type:  
 Time Domain (Transient)  
 Run to time: 20ms  
 Maximum step size: 1us  
 Parts:  
 OPAMP/CLASS  
 VSIN/CLASS

- The difference amplifier rejects noise (Interference Source) and amplifies a source (Microphone)
- Run a Time Domain (Transient) with three Voltage/Level Markers, and one pair of Voltage Differential Markers.
- Label each waveform and explain the shape and amplitude
- Why is the Microphone amplified, and the Interference suppressed?
- Change R1 to 15k and observe the waveforms, what is the circuit doing in this case?


# PSpice Tips

- To display more than one plot at a time:  
**Plot>Add Plot to Window**
- To move traces to different plots: Select the trace name on the current plot, type **CTRL C** ( to copy ), click on the new plot, and type **CTRL V** (to paste ).
- To draw an arrow on the plot :  
**Plot>Label>Arrow**


# Why Does the Noise Cancel?

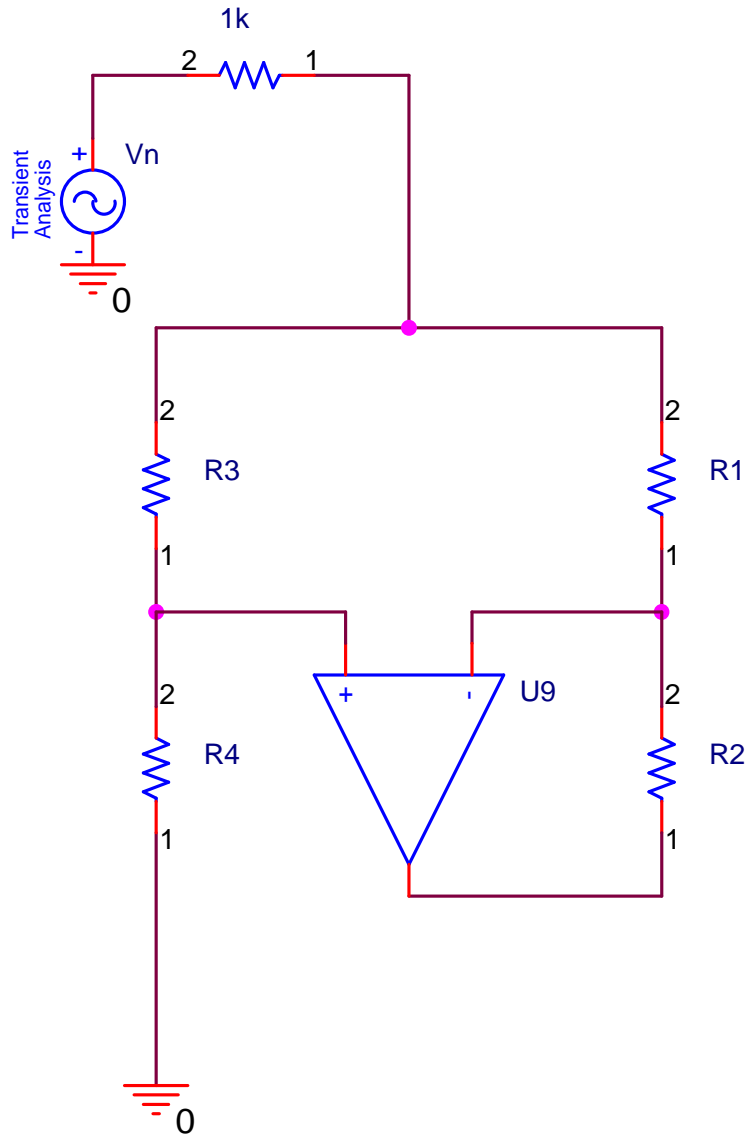

# Why is $V_{BA}$ Amplified?

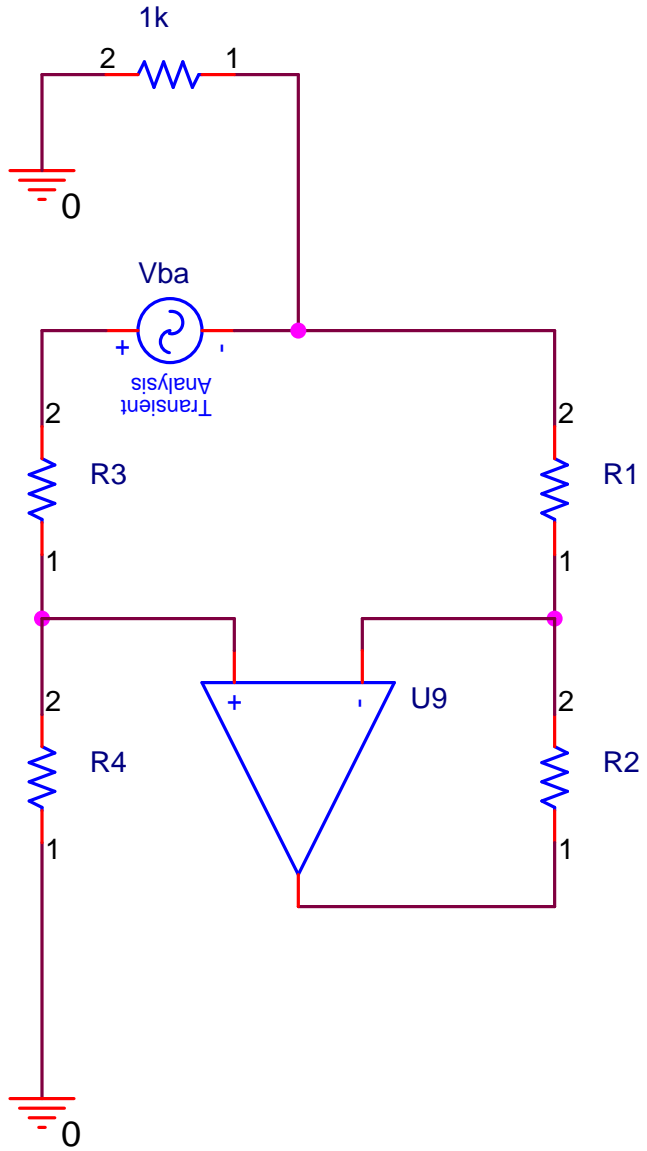

# PART 4: Light Meter

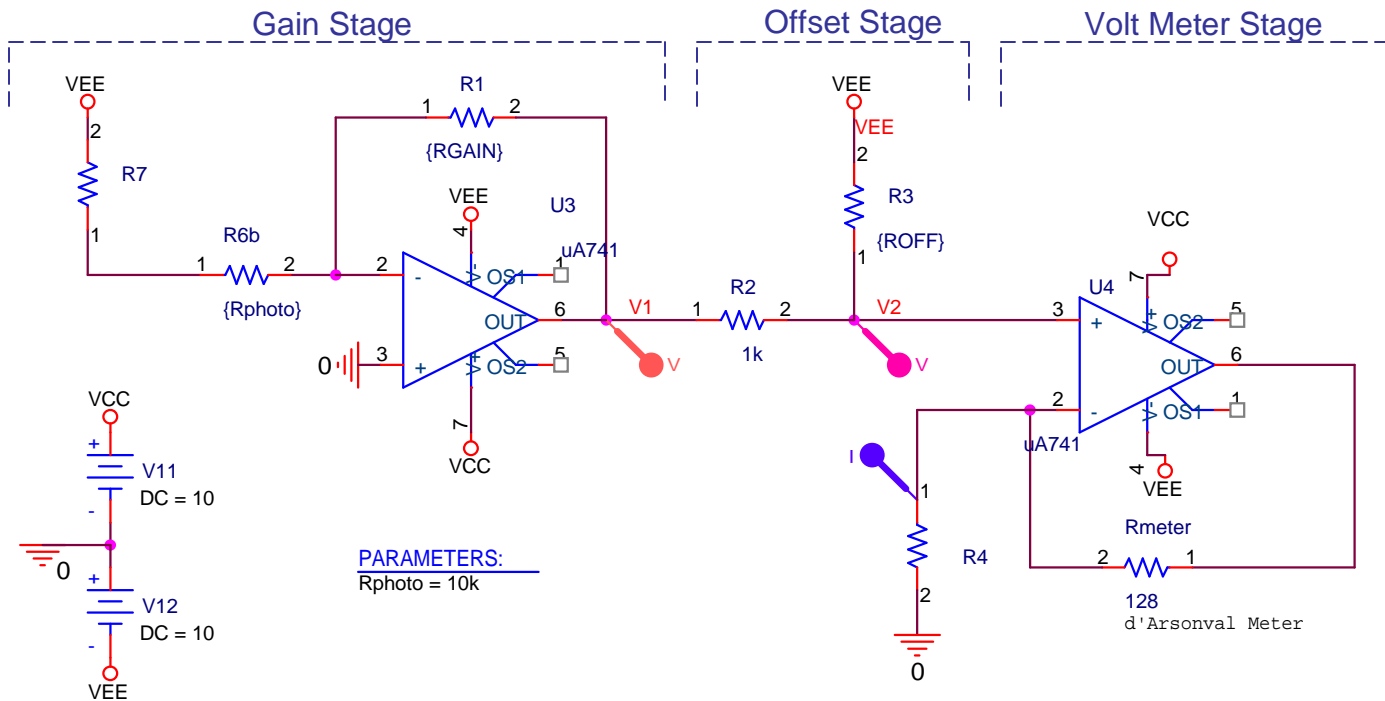

## PSPICE:

Analysis Type:  
DC Sweep

Global Parameter:  
Rphoto

Sweep Type:  
Logarithmic

Start Value: 100Ω  
End Value: 10k Ω

Points/Decade: 50

## Design Specs:

|             | <u>Light</u> | <u>Dark</u> |
|-------------|--------------|-------------|
| $R_{PHOTO}$ | 400          | 10k         |
| $V_2$       | 8V           | 0V          |
| Meter       | 1            | 0           |

- (**Don't forget to answer this**) What is the input resistance of the Volt Meter stage? Compare with the d'Arsonval voltmeter designed in lab 2.
- Follow the steps on page 6 of the Lab handout to design the light meter.
- Check the design with a DC sweep of  $R_{PHOTO}$ . Print one graph of  $v1$  and  $v2$  Vs.  $R_{PHOTO}$ , and one graph of  $I_{METER}$  Vs.  $R_{PHOTO}$