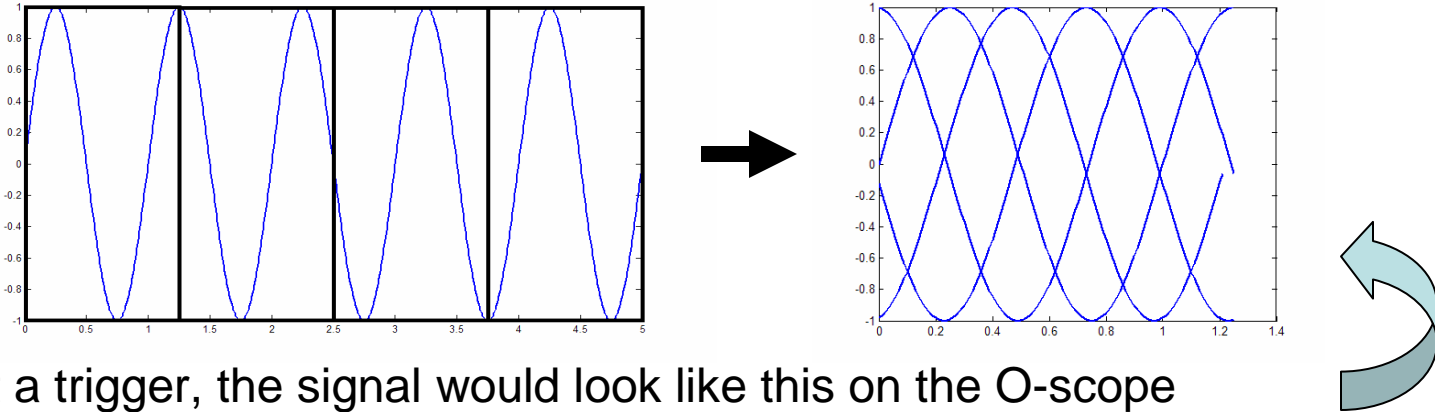


Lecture 5 Goals:


- Lab Skills
 - Oscilloscope Triggering
- Analyze the Step response of a RC Circuit
 - PSpice: Placing the Cursor at a specific point
- Design a Timer Circuit
- Design a Integrating Op-Amp

Oscilloscope Triggering

- The trigger level tells the oscilloscope when to start sweeping out the trace



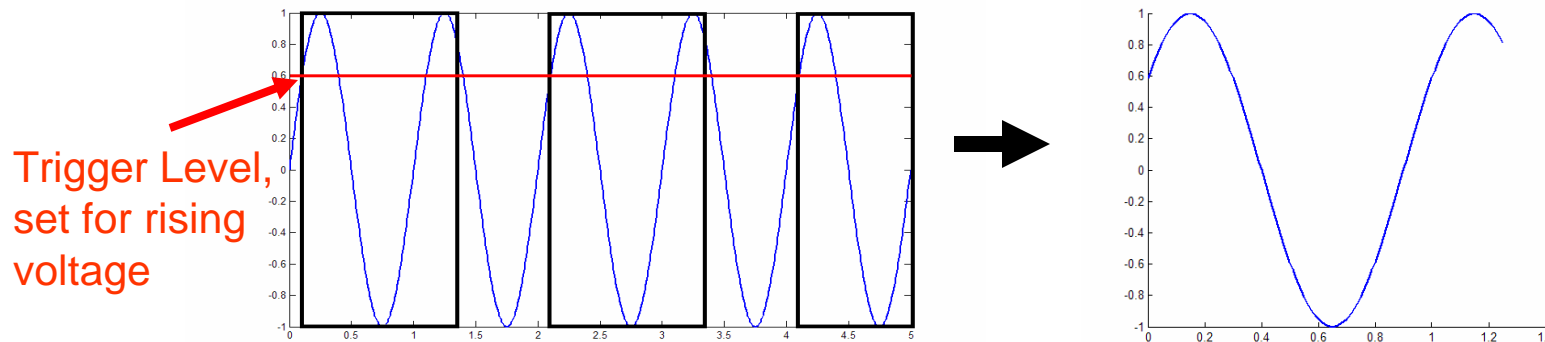
- Without a trigger, the signal would look like this on the O-scope



Trigger Level,
set for rising
voltage


- A trigger level makes the graph look more consistent.
- The trigger can be CH1, CH2, or an external source.
- The level can be adjusted, and set for either rising or falling voltage.

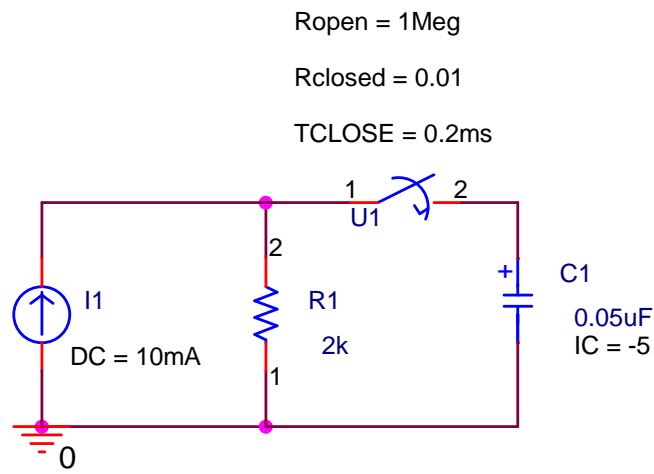PART 1: Response of an RC circuit to a Step Input




PSPICE:	
Analysis Type:	Time Domain (Transient)
Run to time:	1ms
Maximum step size:	1us
New Parts:	Parameters:
Sw_tClose/EVAL	TCLOSE, Rclosed, Ropen
C/CLASS	IC

- Find: $V(t)$, $I_C(t)$, and $I_R(t)$ for $t \leq t_0^-$ and $t \geq t_0^+$ in terms of $\{I, R, C, V_0, t_0\}$. Use the FIFE equation.
- Run a Time Domain (Transient). Plot $V(t)$, $I_C(t)$, and $I_R(t)$, and mark the curves at $t = 0.3\text{ms}$.
- Calculate your equations for $t = 0.3\text{ms}$. Troubleshoot if you values do not match PSpice (i.e. adjust switch parameters, check ckt, TI-89...)
- Based on how capacitors behave (effective characteristics), justify the results of $V(t)$, $I_C(t)$, and $I_R(t)$ at $t = t_0^+$ and $t = \text{infinity}$.

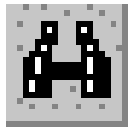

Search Commands

- The cursor can be positioned to a specific x value, or a specific y value using cursor search.
- First click the cursor search button 
- Select a cursor to move.

For a specific x value:



The dialog box has a blue title bar with the text "Search Command". Below the title bar is a text input field containing "search xvalue (x)". Underneath the input field, there is a label "Cursor To Move:" followed by two radio buttons: "1" (which is selected) and "2". At the bottom of the dialog are two buttons: "OK" and "Cancel".

For a specific y value:




The dialog box has a blue title bar with the text "Search Command". Below the title bar is a text input field containing "search level (y)". Underneath the input field, there is a label "Cursor To Move:" followed by two radio buttons: "1" (which is selected) and "2". At the bottom of the dialog are two buttons: "OK" and "Cancel".

NOTE: the search starts from the current position and moves forward (by default) additional commands can change the search direction:

search [forward/backward] [xvalue/level] [(value)]

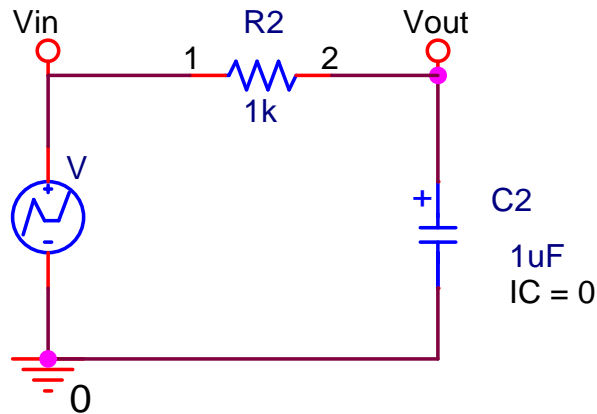
PART 2: Response of an RC circuit to a Pulse Input



PSPICE:	
Analysis Type:	Time Domain (Transient)
Case:	3τ 5τ
Run to time:	9ms 15ms
Maximum step size:	1ms 1ms
New Parts:	Parameters:
VPWL/SOURCE	t1, t2, t3, t4, t5, v1, v2, v3, v4, v5
-OR- VPULSE/SOURCE	V1, V2, TD, TR, TF, PW, PER

- Run a Time Domain (Transient) with the voltage source setup to have a pulse width of 3 ms. Make sure initial cap voltage is 0V. Add a trace to the plot for Vin and Vout. Mark Vout at 6ms. **Print 2 copies and keep one for the lab experiment.**
- What % of its final value does Vout rise to?
- Adjust your voltage source for a pulse width of 5 time constants (5ms). Repeat transient and find % final value.

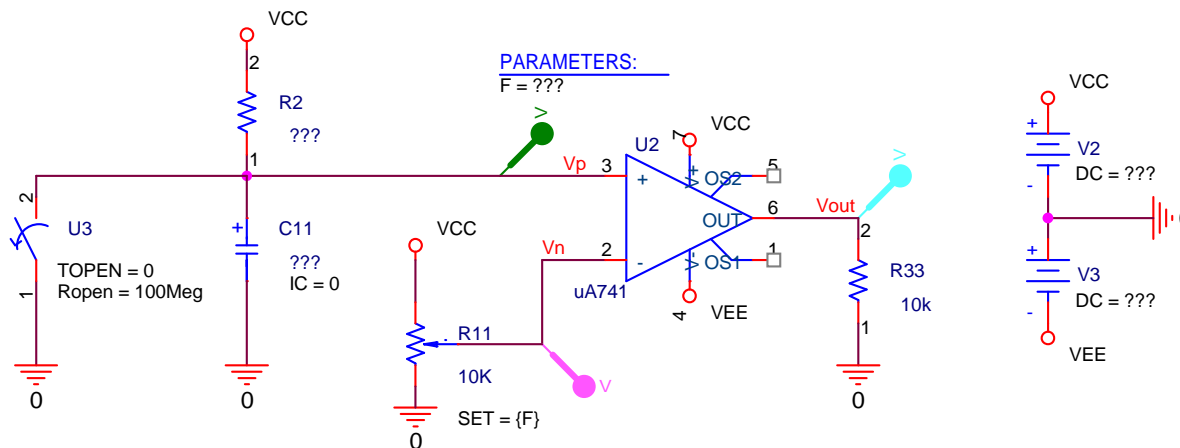PART 3: RC Timing Circuit with Comparator



PSPICE:

Analysis Type:
Time Domain (Transient)

Run to time:
15s

Maximum step size:
10ms (Increase to shorten simulation time)

New Part:
Sw_tOpen/EVAL


Parameters:
TOPEN, Rclosed, Ropen

- Design the circuit such that at $t = 10$ seconds V_{out} changes from 0 V to 5 V.
- First find the capacitor voltage as a function of time. Set the time constant to an appropriate value using standard capacitors and resistors
- Adjust the pot setting F such that $V_n = V_p$ at $t = 10$ seconds.
- Make sure T_{OPEN} is at least 100 M Ω . Run a Time Domain (Transient) with voltage probes at V_p , V_n , and V_{out} . Adjust V_{cc} and V_{ee} such that V_{out} is as close to 0 and 5 V as possible. **Mark V_{out} at the 0 V case, 5 V case, and the 12 second transition**

Design Specs:	
$V_{OUT} = 0 \pm 0.1 \text{ V}$	$\text{for } t < 10 \text{ sec}$
$V_{OUT} = 5 \pm 0.1 \text{ V}$	$\text{for } t \geq 10 \text{ sec}$
<i>Transition time:</i>	$10 \pm 0.1 \text{ sec}$

NOTE: PSpice ver. 15.7 will complain that too many components are being used. Removing the switch, and setting the CAP IC = 0 will fix the problem

PART 4: Integrating Op-Amp Circuit

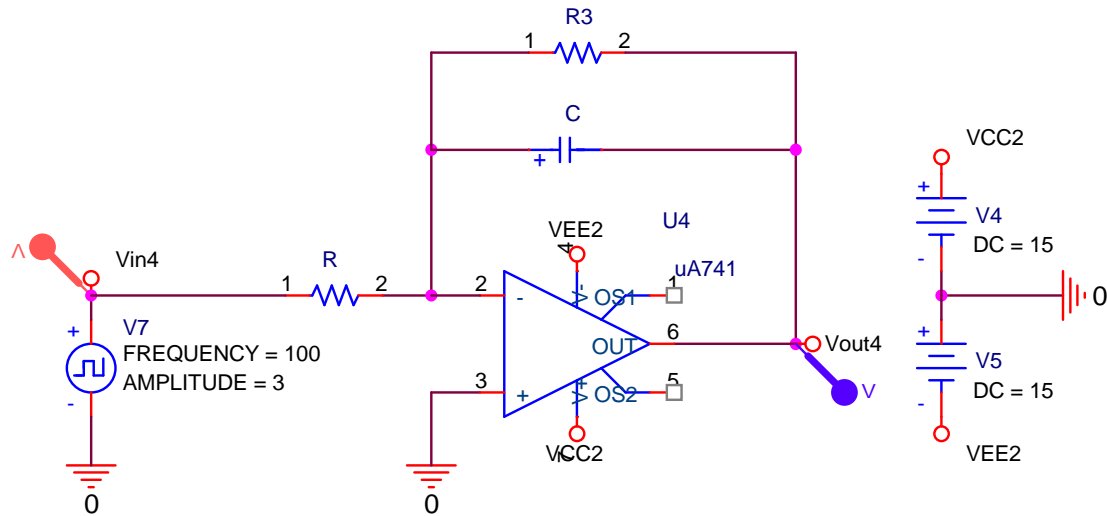

PSPICE:

Analysis Type:

Time Domain (Transient)

Run to time:

20 cycles of output

Maximum step size:

1us (Increase to shorten simulation time)

Check "Skip initial transient solution"

New Part:

Vsq/CLASS

Parameters:

FREQUENCY, AMPLITUDE

- Design R and C such that Vout has a peak to peak voltage of $6 V_{P-P}$. Use standard values.
- Figure out how long to run a transient such that 20 cycles of Vout is shown.
- Find a value for R_f that effectively removes the drift while keeping Vout within 200mV of $6 V_{P-P}$.
- Run another transient long enough to see the drift settle down, **mark** this settling down time (t_s) and its corresponding V_{P-P} .

Design Specs:

$V_{OUT} = 6 \pm 0.2 V_{P-P}$ Sawtooth Wave

Remove drift after a settling down time